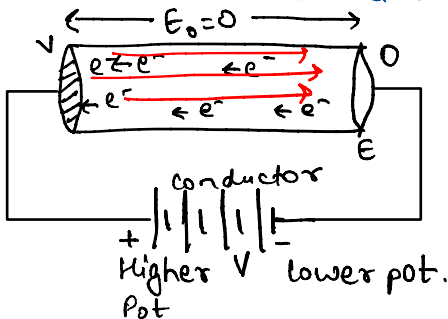


12th BOARD HACKER

Current Electricity

Electric current - Rate of flow of charge through wire

- conductors $\boxed{e^- e^- e^-}$ free e^-
 \oplus charges are fixed in conductor
- current will be due to e^- only
- when there is no battery all e^- are in random motion
- no net current in conductor
- when battery is apply, there is force on e^- & they start moving towards (+) terminal.



$$I = \frac{\text{charge flow}}{\text{time}} = \frac{dq}{t} \quad \text{unit} = A$$

$$\text{dimension} = [A]$$

$$I = \frac{dq}{dt}, \quad \int dq = \int I \cdot dt$$

- electric field outside a current carrying conductor is zero but inside a conductor is V/L

- $I = (2 + 3t)A$. charge crossed in first 10 seconds

$$dq = I \cdot dt$$

$$Q_T = \int_0^{10} (2 + 3t) \cdot dt = 2[t]_0^{10} + 3\left[\frac{t^2}{2}\right]_0^{10}$$


$$= 2(10 - 0) + \frac{3}{2}(10^2 - 0^2)$$

$$= 20 + \frac{3}{2} \times 100 = \boxed{170C}$$

- $q = 2t^2$

$$I = \frac{dq}{dt} = \frac{d(2t^2)}{dt} = 4t$$
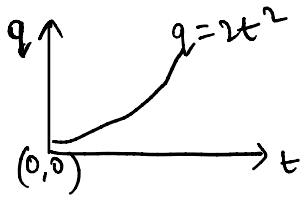
$$I = 4t \quad \text{at } t = 3 \Rightarrow I = 12A$$



Drift velocity & Mobility


- avg. velocity with which e^- drift towards the positive terminal of battery.

- Let there be battery of voltage V is applied across conductor of length ' L '.

- all e^- experience force

$$\vec{F} = -e\vec{E}$$

$$a = -\frac{eE}{m}$$

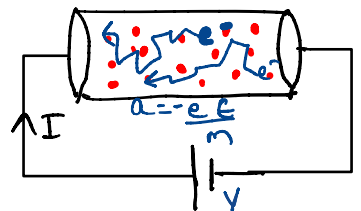


- due to force all e^- experiences collision with atoms & drift towards \oplus terminal of battery.

$$V_{\text{drift}} = \vec{V}_{\text{avg}} = \frac{\vec{v}_1 + \vec{v}_2 + \vec{v}_3 + \dots + \vec{v}_n}{n}$$

$$= \left(\frac{u_1 + u_2 + \dots + u_n}{n} \right) - \frac{e\vec{E}}{m} (t_1 + t_2 + t_3 + \dots)$$

$$V_{\text{drift}} = \vec{V}_{\text{avg}} = -\frac{e\vec{E}}{m} \tau$$

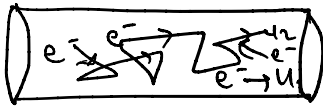τ = avg. time for collision = relaxation time



- e^- are in random motion
- there is no net flow of charge

let e^- have initial velocity $\vec{u}_1, \vec{u}_2, \vec{u}_3, \dots, \vec{u}_n$

$$\vec{u}_{\text{avg}} = \frac{\vec{u}_1 + \vec{u}_2 + \vec{u}_3 + \dots + \vec{u}_n}{n} = 0$$

velocity of all e^- at time t .

$$\vec{v}_1 = \vec{u}_1 - \frac{e\vec{E}}{m} t_1$$

$$\vec{v}_2 = \vec{u}_2 - \frac{e\vec{E}}{m} t_2$$

$$\vec{v}_n = \vec{u}_n - \frac{e\vec{E}}{m} t_n$$

Mobility -

drift velocity attained per unit E .

$$\mu = \frac{V_d}{E} = \frac{eE\tau}{mE} = \frac{e\tau}{m}$$

$m \downarrow \mu \uparrow$
 $\mu_e > \mu_p$
 $\mu_e > \mu_n$

Current density



- ⊕ flow dirⁿ → I (conventional)
- ⊖ flow dirⁿ → opp. to dirⁿ of I.

\vec{J} = current density = amount of current passing per unit area.

$$\vec{J} = \frac{I}{A} \quad \text{unit} = \frac{A}{m^2} \quad \text{Dim} = [AL^{-2}]$$

\vec{J} is a vector quantity (dirⁿ is same as that of current)

∴ other form = $\vec{J} \cdot \vec{A} = I$ $I = JA \cos \theta$


example - $\vec{J} = (2 \times 10^4 \hat{j}) \text{ Am}^{-2}$
find the current through area $\vec{S} = (2\hat{i} + 3\hat{j}) \text{ cm}^2$

solⁿ - $\vec{J} = (2 \times 10^4) \hat{j} \text{ Am}^{-2}$
 $\vec{A} = (2\hat{i} + 3\hat{j}) (10^{-2})^2 \text{ m}^2$
 $I = \vec{J} \cdot \vec{A}$

$$(2 \times 10^4) \times 0 + 3 \times 10^4 \times 2 \times 10^4$$

$I = 6 \text{ A.}$

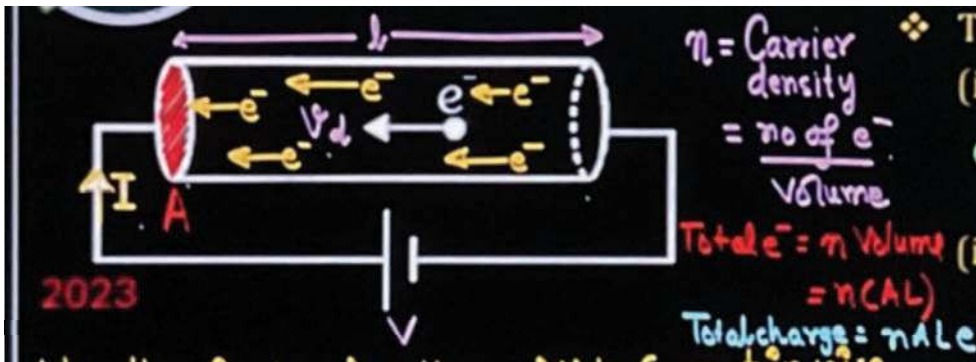Relation between current and drift velocity



when there is a vol of e^- there will be current in wire

$$I = \frac{\text{charge}}{\text{time}} = \frac{nAe}{t}$$

$$I = neAV_d$$

drift velocity.

$$\text{speed} = \frac{d}{t}$$

$$v_d = \frac{L}{t}$$

current
carrier density
e⁻ charge
area of cross-section

$$= \frac{\text{no. of } e^-}{\text{volume}} \rightarrow \text{depends on nature of cond.}$$


* The conductor remains uncharged.

i) It is same along the wire

$$I_1 = I_2$$

$$I = neAV_d$$

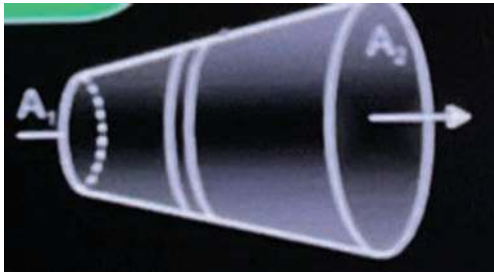ii) Current density, electric field strength, drift velocity are inversely proportional to area. Here $I_1 = I_2$ but $A_1 < A_2$, so $J_1 > J_2$, $E_1 > E_2$, $v_{d1} > v_{d2}$.




conductors of random shape

$$AV_d = \text{const.} \quad J = \frac{I}{A} \text{ (same)}$$

$$\vec{J} = \sigma \vec{E}$$

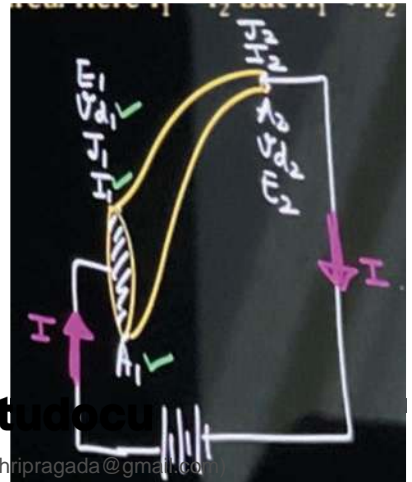- $A_1 > A_2$
- $v_{d1} < v_{d2}$
- $J_1 < J_2$
- $E_1 < E_2$.



Ohm's law, Resistance, Resistivity

↳ when we apply battery of voltage V across a conductor, relation between V & I .

$$E = \frac{V}{L}$$

$$\# I = neAv_d$$

$$I = neA \frac{eE\tau}{m}$$

$$I = \frac{ne^2 \tau A E}{m}$$

$$I = I \left(\frac{mL}{ne^2 \tau A} \right)$$

Resistance, $R = \frac{mL}{ne^2 \tau A}$

length of conductor $\rightarrow R \propto L$
 area of cross section $\rightarrow R \propto \frac{1}{A}$

nature of Mat. $\rightarrow R \propto \frac{1}{n}$

Temp. $\rightarrow R \propto \frac{1}{\tau}$

Ohm's law -

at low & const. temp. $V_{app} \propto I$ through cond.

resistivity - depends on temperature

- temp \uparrow - collision rate \uparrow - time b/w collision

- $\tau =$ avg. time of collision $\downarrow \Rightarrow R \uparrow$.

$$\# R = R_0 (1 + \alpha \Delta T)$$

\downarrow
 R at $0^\circ C$

↳ change in temp.
 ↳ temp. coeff. of resistance

$$R = \frac{\rho L}{A}, \quad \rho = \rho_0 (1 + \alpha \Delta T)$$

Microscopic Ohm's law vector form law

from relation - $\frac{I}{A} = \frac{ne^2 \tau E}{m}, \quad \vec{J} = \frac{\vec{E}}{\rho} \Rightarrow \vec{J} = \sigma \vec{E}$

$\sigma = \frac{1}{\rho} =$ conductivity.

(property of cond by which it opposes flow of current through it) unit = Ω ohm.

$$R = \frac{V}{I} = \left[\frac{ML^2 T^{-2} A^{-2}}{C^2} \right]$$

$$V \propto I$$

$$\Rightarrow V = IR$$


$$R = \frac{V}{I}$$

conductance $\Rightarrow G = \frac{1}{R}$


unit = Ω^{-1} , mho, siemen, S.

Important graphs


ohm's law

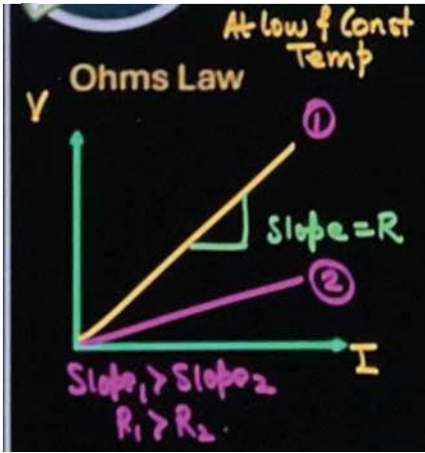

V vs I for diff. temp.

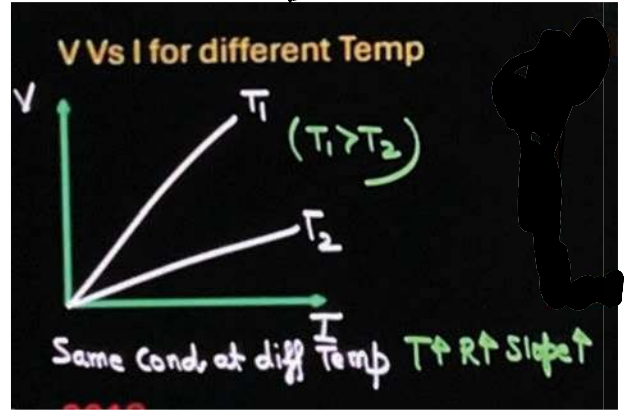

V vs I for non-ohmic resistance

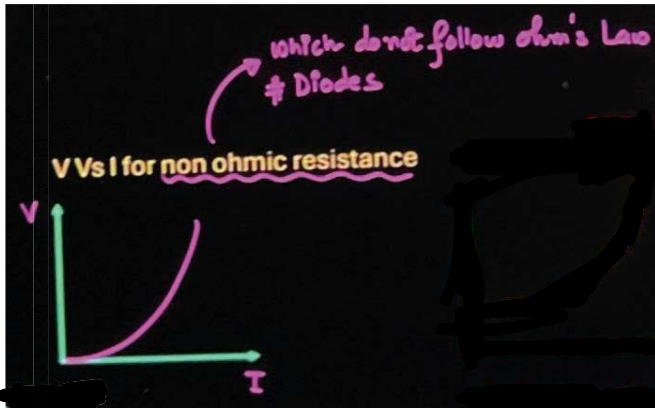

R Vs temp for conductor





R vs T for semiconductor



R vs T for Semiconductor 2019

$R = \frac{mL}{ne^2A}$, Temp ↑ bonds break (↓) e⁻ hole pairs develop (↑)
 $R \propto \frac{1}{n\tau}$ (↑) (↓)
 n dominates over τ, overall (nτ) ↑ hence R_{semi} ↓.

Combination of Cells

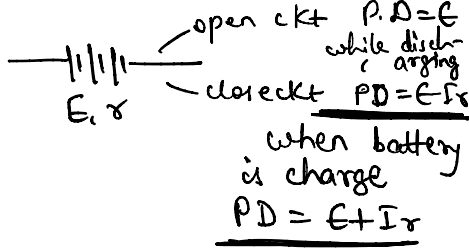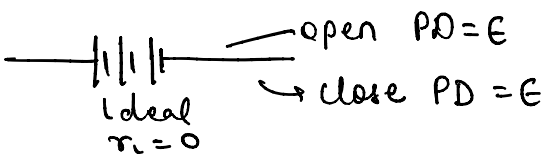

a) Series combination

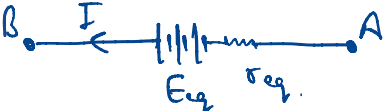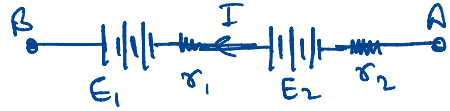

$$V_A - Ir_2 + E_2 - Ir_1 + E_1 = V_B$$


$$E_2 + E_1 - I(r_1 + r_2) = V_B - V_A \quad \text{--- (1)}$$

↳ ①

$$V_A - I r_{eq} + E = V_B$$

$$E_{eq} - I r_{eq} = V_B - V_A \quad \text{--- (2)}$$

b) Parallel combination

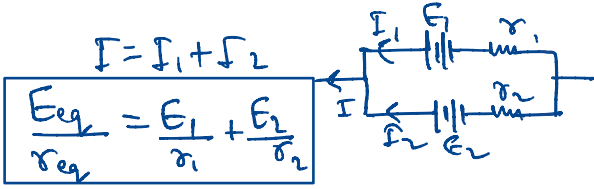

If there are n batteries

$$\frac{E_{eq}}{r_{eq}} = \frac{E_1}{r_1} + \frac{E_2}{r_2} + \frac{E_3}{r_3} + \dots$$



on comparing 1 & 2
 $E_{eq} = E_1 + E_2$ $r_{eq} = r_1 + r_2$

If n batteries +nt

$$E_{eq} = E_1 + E_2 + E_3 + \dots + E_n$$

$$r_{eq} = r_1 + r_2 + r_3 + \dots + r_n$$

In n equal battery

$$E_{eq} = nE \quad r_{eq} = nr$$



n identical batteries
 in parallel.

$$\frac{1}{r_{eq}} = \frac{1}{r} + \frac{1}{r} + \frac{1}{r} + \dots$$

$$\frac{1}{r_{eq}} = \frac{n}{r} \Rightarrow \boxed{r_{eq} = \frac{r}{n}}$$




$$\frac{E_{eq}}{r_{eq}} = \frac{E}{r} + \frac{E}{r} + \dots + n \times \frac{E}{r}$$
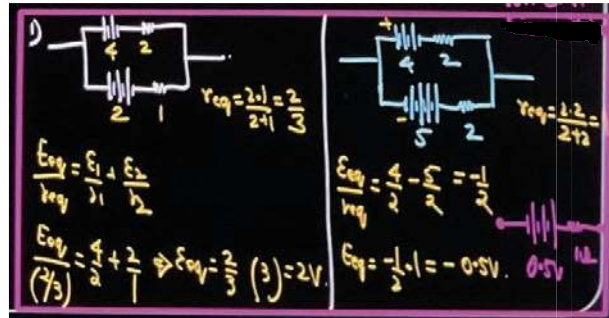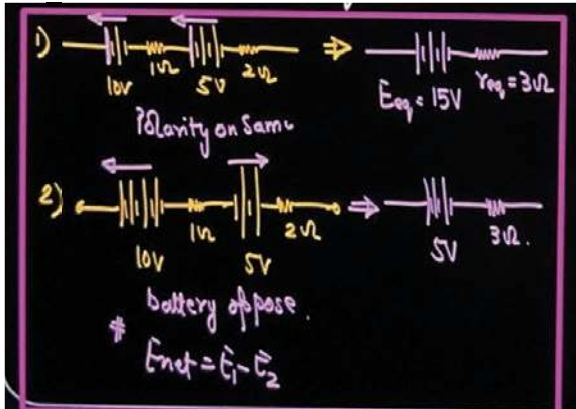
$$\frac{E_{eq}}{r_{eq}} = \frac{nE}{\frac{r}{n}} \cdot r_{eq} = E \cdot n \cdot \left(\frac{r}{n}\right) = E$$



Battery grouping

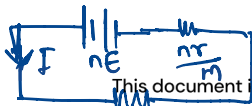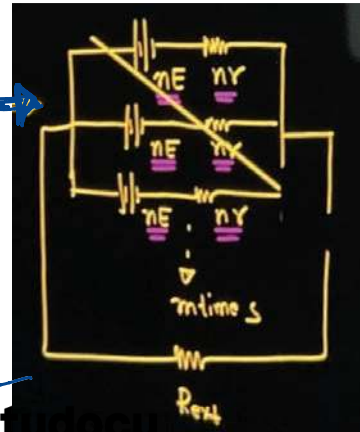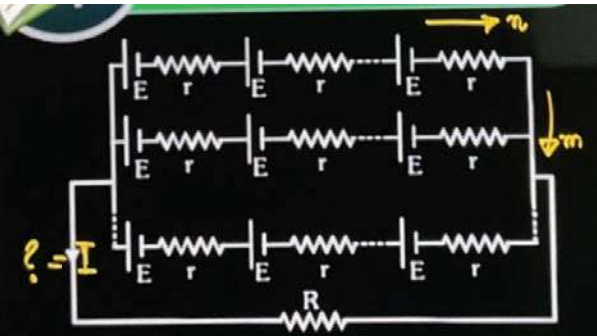n identical batteries in series & m rows
 - find current in R_{ext} .



This document is available on



$$I = \frac{V_T}{R_T} = \frac{nE}{R_e + \frac{nR}{m}}$$

What is the condⁿ for I to be max^m -

$$I = \frac{nE}{mR + nR}$$

$I = \text{max}^m$
deno. \rightarrow minⁿ

$$mR + nR = (\sqrt{mR})^2 + (\sqrt{nR})^2$$

$$\text{min}^n = (\sqrt{mR})^2 + (\sqrt{nR})^2 + 2\sqrt{mRnR} - 2\sqrt{mRnR}$$

$$= (\underbrace{\sqrt{mR} - \sqrt{nR}}_{=0})^2 + 2\sqrt{mRnR}$$

Condⁿ, $\sqrt{mR} = \sqrt{nR}$
 $mR = nR$
 $R = \frac{nR}{m}$

When R_{ext} of ckt is equal
 net internal resistance
 of batteries
 $I \rightarrow \text{max}^m$.

Kirchoff's Laws


first law or junction law
 (Kirchoff's current law)
 (KCL)

Second law or
 Funcⁿ law
 (Kirchoff's Voltage law)
 (KVL)

The total current entering a junⁿ or a node is equal to charge leaving the node as no charge is lost

The voltage around a loop equals the sum of every voltage drop in the same loop for any closed network and equal zero

Based on charge conservation,

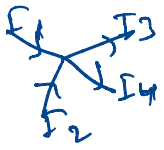

- net current at any junⁿ = zero
 - sign $I_{incomi} = -ve$
 $I_{outgoi} = +ve$
- $$-I_1 - I_2 + I_3 + I_4 = 0$$

Conservation of Energy.

$$\sum V_{all} = 0$$

$$V_1 + V_2 + V_3 = 0$$

Sign Convention:


E (battery) $+E$

$-IR$ (resistor)

$+IR$ (resistor)

When \rightarrow dir of I

Wheatstone Bridge

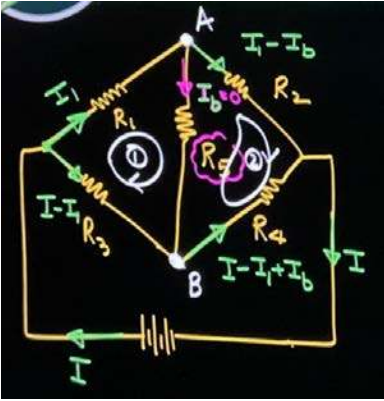

Combination of 5 Resistance as shown in which if there is no current in bridging Resistance

$$\rightarrow V_A = V_B \rightarrow I_b = 0$$

$$\rightarrow \frac{R_1}{R_2} = \frac{R_3}{R_4}$$

\rightarrow this condⁿ is called a balanced WSB

KVL for loop 1 $+R_3(I-I_1) - I_1 R_1 - I_b R_5 = 0$

KVL for loop 2 $+I_b R_5 - (I-I_1)R_2 + (I-I_1+I_b)R_4 = 0$

In balanced condⁿ $I_b = 0$

$$R_3(I-I_1) = I_1 R_1$$

$$R_4(I-I_1) = I_1 R_2$$

Ratio $\Rightarrow \frac{R_1}{R_2} = \frac{R_3}{R_4}$

Meter Bridge

— working principle = balanced condⁿ of WSB.

applicⁿ of WSB = to find value of unknown resistance

\rightarrow It has a wire of length '1m'

when there is no deflection in Jockey ($I_g = 0$) WSB is balanced.


$$\frac{R_k}{R_u} = \frac{l}{100-l} \Rightarrow R_k = R_u \frac{(100-l)}{l}$$

R_k = Known resistance


R_u = unknown resistance

end correction

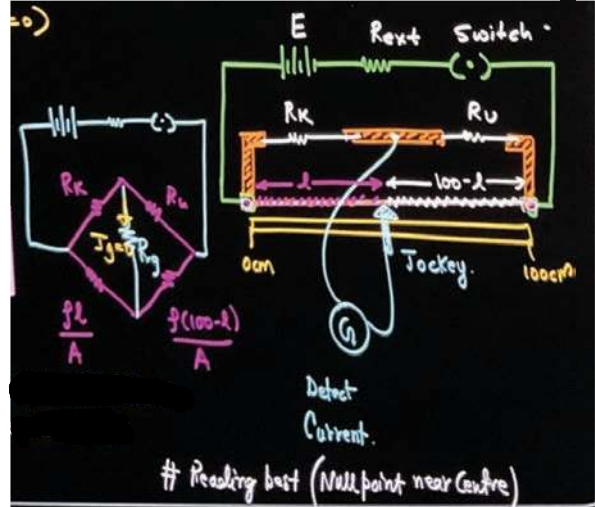wire endings at screw give additional resistance if we consider that resistance also, it is called end correction.



Heat

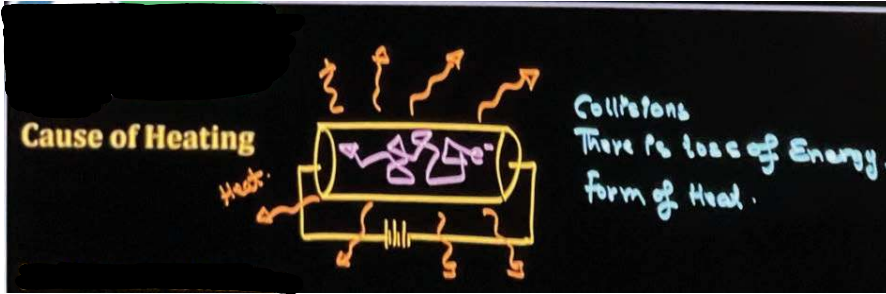

Joules law of heating — when a current I is made to flow through a ohmic resistance R for time t , heat Q is produced such that

$$\begin{aligned} \text{heat} &= I^2 R t \\ &= \frac{V^2}{R} t \\ &= V I t \end{aligned}$$

heat produced in a conductor does not depend upon the direction of current.

Power through bulbs

Power: Rate of doing work

$$P = \frac{\text{Heat}}{t}$$

$$P = VI$$

$$= \frac{V^2}{R}$$

$$= I^2 R$$

unit = Watts.
Commercial unit = Kwh.

Series Combination $I = \text{Same}$, ($P = I^2 R$) better

Parallel Combination $V = \text{Same}$, ($P = \frac{V^2}{R}$) better.

Bulb:

$$P_0 = \frac{V_0^2}{R}$$

$$R_{\text{bulb}} = \frac{V_0^2}{P_0}$$

↓
does not vary.

More is Power in ckt → More is the Brightness



$$P_{\text{ckt}} = \frac{V_{\text{applied}}^2}{R} = \frac{V^2}{R} P_0$$

$$P_{\text{ckt}} = \left(\frac{V}{V_0}\right)^2 P_0$$

$V < V_0$ Brightness ↓
 $V = V_0$ $P = P_0$
 $V > V_0$ Brightness ↑

2020
Tungsten filament
 • High Melting point.
 • Not Easily oxidized
 • R does not vary Rapidly Temp.



$P_0 = \text{Rated Power}$
 $V_0 = \text{Rated Voltage}$

Jo us par likha hai.
Ex: - 100 watt, 220v.
220v milega tab 100 watt power hoga.

Brightness/Power ⇒ Replace all bulbs by $R = \frac{V^2}{P_0}$ then find Power in ckt, P₁ BT, P₂ & P₃.

(a) Series combinations 2024, 2019



$$R_s = R_1 + R_2$$

$$\frac{V^2}{P_s} = \frac{V^2}{P_1} + \frac{V^2}{P_2}$$

$$\frac{1}{P_s} = \frac{1}{P_1} + \frac{1}{P_2}$$

(b) Parallel Combination 2023, 2019



Parallel Comb.

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{P_p}{V^2} = \frac{P_1}{V^2} + \frac{P_2}{V^2}$$

$$P_p = P_1 + P_2$$