


→ Transistors are widely used in digital logic circuits and switching applications, in these applications the voltage levels periodically alternate between a low and high voltage such as 0V & 5V

→ In switching applications the transistor operates in either cutoff region (or) saturation region. Consider it to be connected in ^{common emitter} CE configuration.

→ when the input is high [5V] base current flows and hence transistor is operated in saturation region. In this situation transistor acts as a closed switch.

→ when the input is low the base & collector current is 0. Hence transistor is operated in cutoff region and acts as an open switch.

Transistor Current Components (Mid)

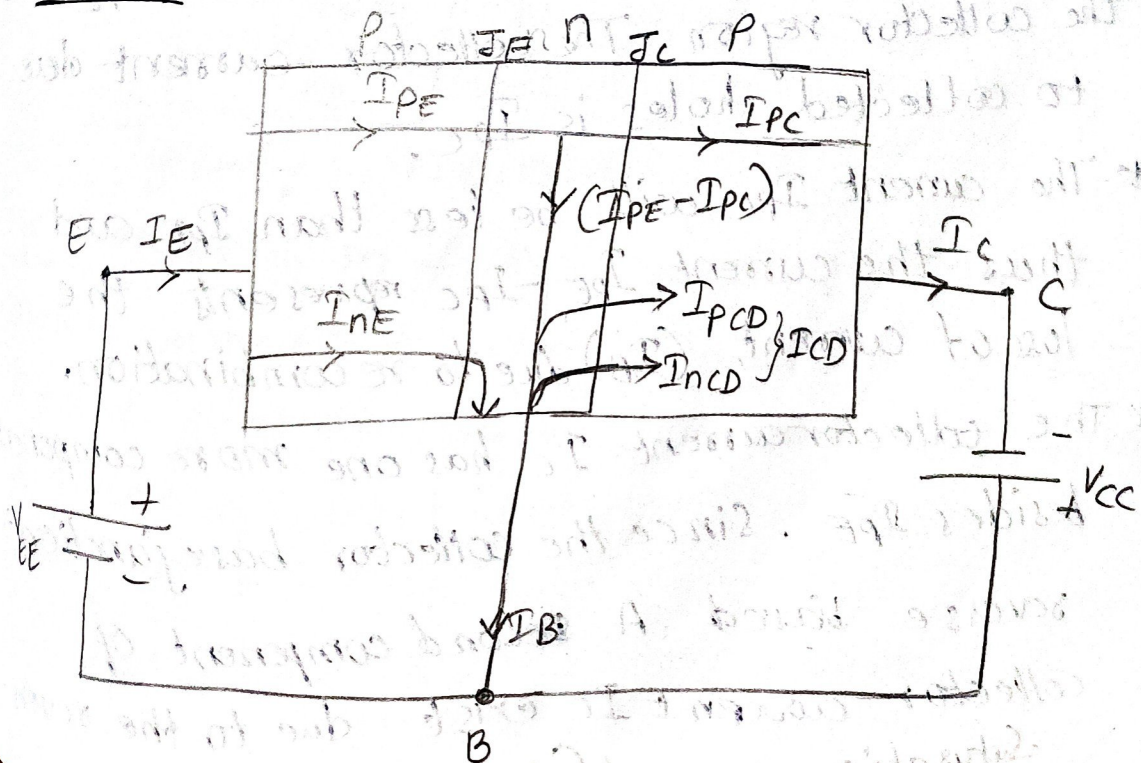

Q.1

* Consider a pnp transistor in which emitter base junction is forward biased and but collector base junction is reverse biased.

* The emitter current I_E has 2 currents

i, Hole injected current (I_{pE}) due to holes crossing from emitter to base.

ii, Electron injected current (I_{nE}) due to electrons injected from base to emitter.

* Since the emitter region is heavily doped compare to base region, the hole current I_{pE} is always much larger compare to e^- current I_{nE} the total emitter current I_E is $I_{pE} + I_{nE} \rightarrow \text{①}$

* Since the base region is very thin and has very low doping level only a few of injected holes of I_{pE} are lost due to recombination. Thus most of injected holes in current I_{pE} reach the collector region. The collector current due to collected holes is I_{pC} .

* The current I_{pC} will be less than I_{pE} and thus the current $I_{pE} - I_{pC}$ represents the loss of current (I_B) due to recombination.

* The collector current I_C has one more component besides I_{pE} . Since the collector base junction is reverse biased. A second component of collector current I_C exist due to the reverse saturation current (I_{C0}).

* The thermally generated holes in base region move to collector region and constitute a current component (I_{pco}). Similarly, thermally generated e^- in collector region moves to base region and constitute a current component I_{nco} . \therefore
 \therefore The total Reverse saturation current.

$$I_{co} = I_{pco} + I_{nco} \quad \rightarrow (2)$$

* So, the total collector current $I_c = I_{pc} + I_{co} \rightarrow (3)$

* As, a standard convention all the currents entering into the transistor are taken to be +ve.

* The current flowing out is taken as -ve.

Hence, In a pnp transistor I_E is positive &

I_c and I_B are -ve.

* Emitter injection ratio: The ratio of whole current to the total emitter current is known as emitter injection ratio.

$$r = \frac{I_{pE}}{I_E}$$

Typically, $r = 0.995$

Base transportation factor: The ratio of injected carrier current at collector junction to the injected carrier current at emitted junction is known as Base transportation factor.

Denoted by β' .

$$\beta' = \frac{I_{pC}}{I_{pE}} \quad \text{Typically, } \beta' = 0.995$$

Current Gain: The large signal current gain

' α ', is defined as $I_C = \alpha I_E$

Since I_C is always less than I_E , α has a less value less than unity ranging from 0.90 to 0.995

from eqn (3) $I_E = I_C + I_{CO}$

$$I_C = \alpha I_E + I_{CO}$$

$$\alpha I_E = I_C - I_{CO}$$

$$\alpha = \frac{I_C - I_{CO}}{I_E}$$

Transistor Equation:

* In active region of the transistor, the emitter is forward biased and collector is reverse biased. The Generalized expression for the collector current I_C for collector junction voltage V_C and Emitter current I_E .

$$I_C = \alpha I_E + I_{CO} (1 - e^{V_C / V_T}) \rightarrow (1)$$

* If V_C is -ve and $|V_C|$ is very large compared with V_T . The above eqn reduces the

$$I_C = \alpha I_E + I_{CO} \rightarrow (2)$$

We know, $I_E = I_B + I_C$

sub I_E value in eq (2)

$$I_C = \alpha (I_B + I_C) + I_{CO}$$

$$I_C = \alpha I_B + \alpha I_C + I_{CO}$$

$$I_C - \alpha I_C = \alpha I_B + I_{CO}$$

$$I_C (1 - \alpha) = \alpha I_B + I_{CO}$$

$$I_C = \frac{\alpha I_B + I_{CO}}{1 - \alpha}$$


$$I_C = \frac{\alpha I_B}{1 - \alpha} + \frac{I_{CO}}{1 - \alpha}$$

$$\text{let } \beta = \frac{\alpha}{1 - \alpha}$$

$$I_C = \beta I_B + (1 + \beta) I_{CO}$$

Increasing the signal strength in terms of i, v is called Amplification

Transistor as an Amplifier;

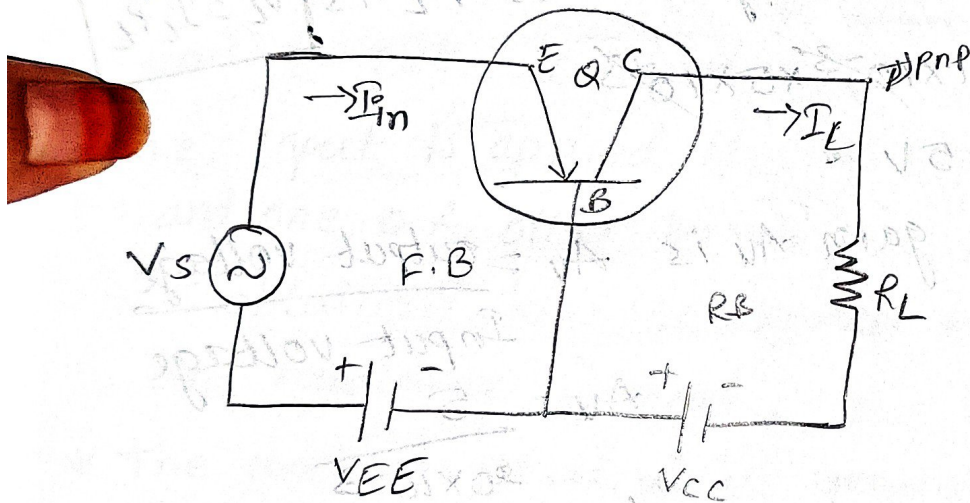

- * Consider a pnp transistor in active region of operation the AC signal source (V_s) which is to be amplified is connected at input circuit.
- * The load resistor R_L is connected in output circuit and amplifier o/p is taken across R_L
- * The emitter base junction is forward biased hence the input resistance R_i of circuit is small, the order 10Ω to 100Ω only.
- * The collector base junction is reverse biased hence the output resistance R_o of circuit is very high the order of $50k\Omega$ to $1m\Omega$

* The amplifying action of a transistor can be explained by taking a simple example assume $R_i = 20 \Omega$, $R_o = 100 k\Omega$,

$$V_s = 20 mV, R_L = 5 k\Omega$$

$$\text{Input current } I_{in} = \frac{V_s}{R_i} = \frac{20 \times 10^{-3} V}{20} = 1 mV.$$

$$\text{We let } I_L \approx I_{in} \alpha$$

* In a transistor α is always equal to '1'

$$\therefore I_L = I_{in}$$

* The output voltage across R_L is $V_L = I_L R_L$

$$V_L = 1 \times 10^{-3} \times 5 \times 10^3$$

$$V_L = 5V$$

* The voltage gain A_v is $A_v = \frac{\text{output voltage}}{\text{Input voltage}}$

$$A_v = \frac{5}{20 \times 10^{-3}}$$

$$A_v = \frac{5 \times 10^2}{20}$$

$$A_v = 2.5 \times 10^2$$

$$A_v = 250 V$$


* Thus, the input voltage is amplified by 250 times.

* BJT's can be well used for amplification of small AC signals. This is possible because the input circuit has low resistance and output circuit has high

Transistor Configuration


- * A transistor has 3 terminals namely emitter, base and collector.
- * But when a transistor is to be connected in circuit we need four terminals, two terminals for input and two terminals for output.
- * This difficulty is overcome by making one terminal of transistor to both input and output terminals.
- * The input is applied b/w the common terminal and one of other terminals, the output is obtained b/w the common terminal and remaining terminal.
- * The common terminal is generally grounded.
Hence there are 3 transistor configurations
 - 1) Common base configuration
 - 2) " emitter "
 - 3) " collector "
- * In all configuration the emitter junction is forward biased and collector junction is reverse biased, is called Active region.

Common Base Conf.

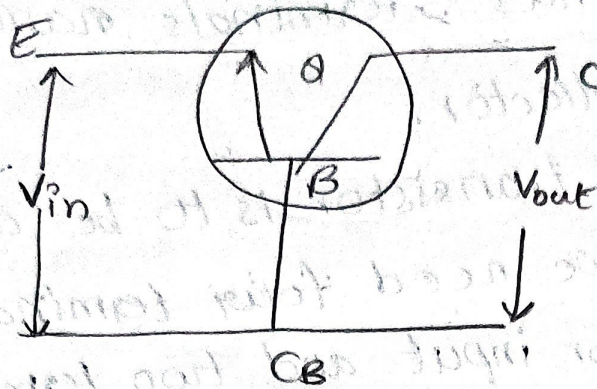


* In CB conf., the transistor is connected with a base as common terminal. The input is applied b/w base and emitter terminals and the output is taken between the collector and base terminals.

Common emitter conf.

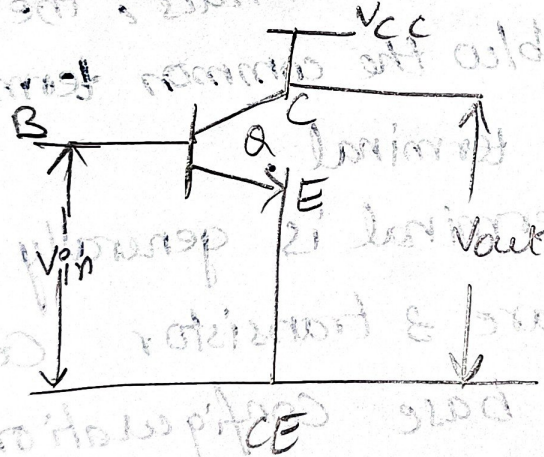

* In CE conf., the transistor is connected with a emitter as a common terminal. The input is applied b/w the base and emitter terminals and the o/p is taken b/w collector & Emitter terminals.

Common Collector Configuration

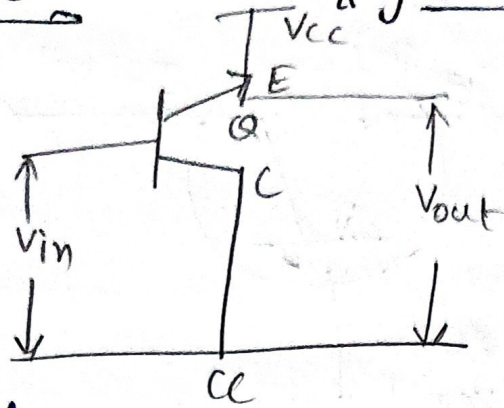

* In CC confi. - the transistor is connected with a collector as common terminal the input is applied b/w the base and collector terminals and o/p is taken b/w the collector and emitter terminals.

Transistor characteristics

* Def: Many details about a transistor can be studied with help of curves which relate the transistor current and voltages.


* These curves are known as static chara... curves.

* The two sets of characteristics which completely describe the static operation of the transistor are input characteristics and output chara...

* high light The input chara... are plotted between the input voltage and input current at constant output voltage.


* The output chara... are plotted between the output voltage and output current at constant input current.

CB Configuration:

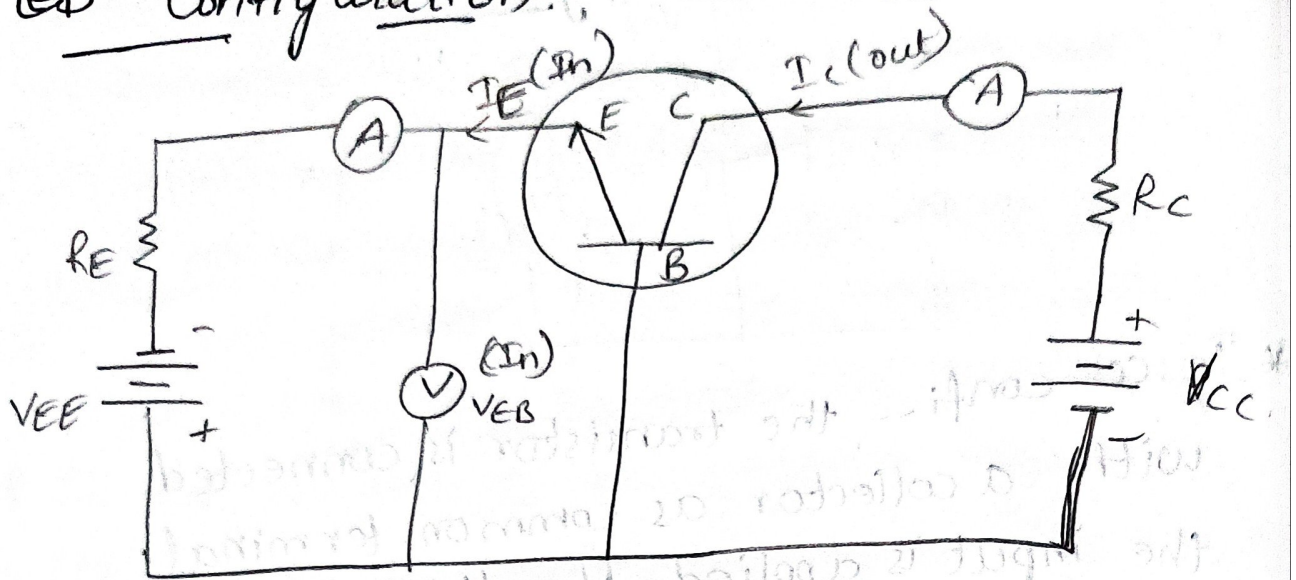

Input characteristics:

- * The input characteristics in CB configuration are plotted between the input voltage that is ' V_{EB} ' and input current i.e., ' I_E '. For constant output voltage i.e., ' V_{CB} '.
- * When $V_{CB} = 0$, the output circuit will not be present and since the emitter-base junction is forward biased, the transistor behaves as a forward biased diode. So, the emitter current increases exponentially.

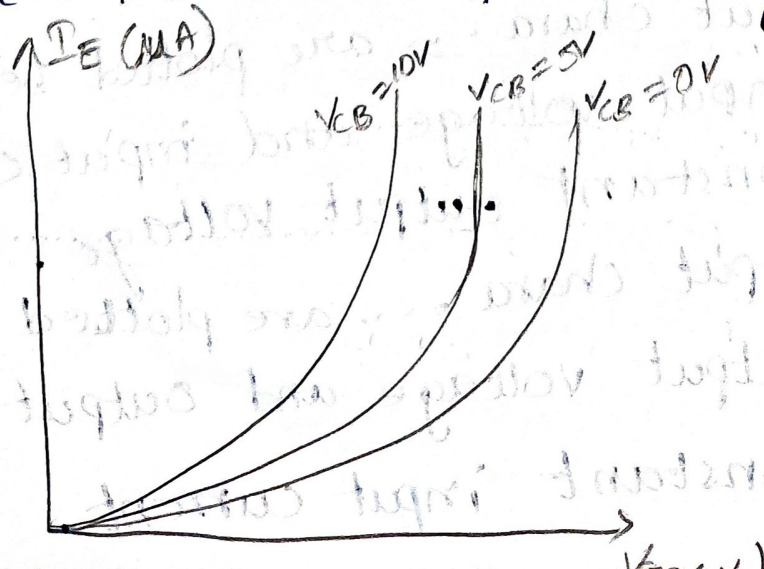


* When V_{CB} is increased for higher fixed values the width of base region decreases and thus emitter current further increases. Thus, the curve shifts towards the left.

Early Effect (or) base width modulation;

- * When the applied reverse voltage increases the width of depletion region at collector junction increases.
- * The depletion region penetrates deeper into the base region thus, the effective base width decreases.
- * The dependency of base width on collector to base voltage is known as early effect (or) base width modulation.

Output characteristics;

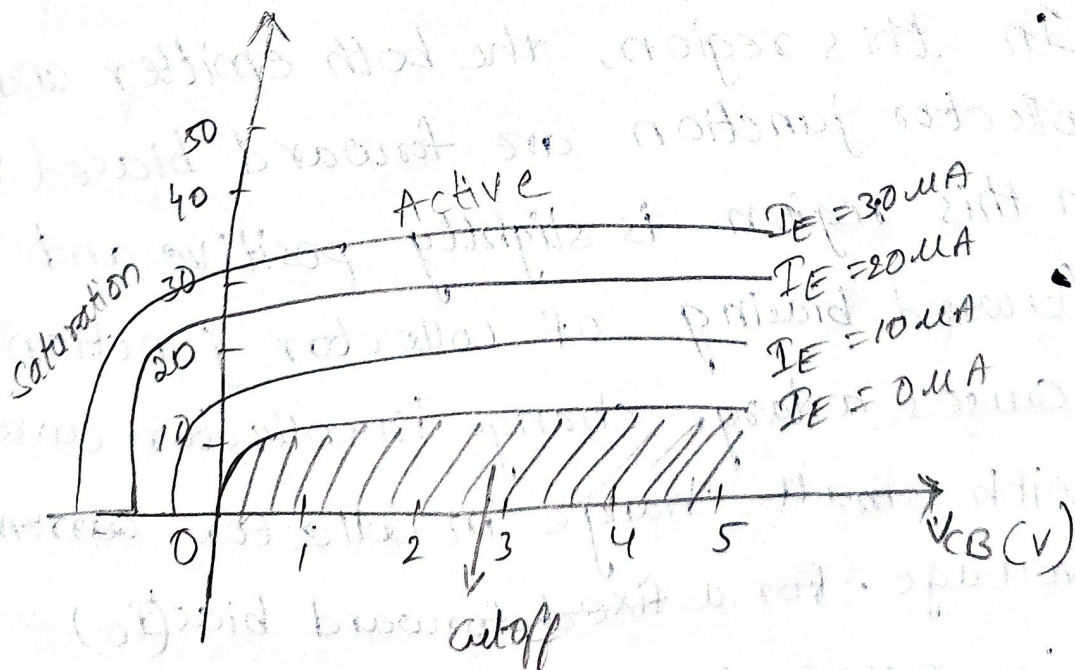

* The CB output characteristics are plotted between output voltage that is collector base voltage and output current i.e., collector current ' I_c '. For, constant input current that is emitter current.

* The output characteristics of transistor is done in three operating regions.

1. Active Region:

In this region, the emitter junction is forward biased and the collector junction is reverse biased. For $V_{CB} > 0$, the characteristics are essentially flat i.e., I_c is independent of V_{CB} . In this region, $I_c \approx I_E$ and $\alpha = 1$

2. Saturation region:

In this region, the both emitter and collector junction are forward biased V_{CB} in this region is slightly positive and forward biasing of collector junction causes a large change in collector current with small change in collector current voltage. For a fixed forward bias (I_c) increases exponentially with voltage.

3) Cut-off region:

In this region, the both emitter and collector junction are reverse biased. Hence the collector current I_c flows even when the emitter current $I_E = 0$. This is due to the collector leakage current ' I_{co} '. This region is below and to the right of $I_E = 0$ characteristic curve.

punch through (or) reach through

According to early effect, the width of depletion region at collector junction decreases with increasing the collector junction voltage.

* As V_{CB} increases, the depletion region penetrates deeper into the base, At the particular level of V_{CB} the effective base width is equal to 0 as result the emitter and collector are effectively shorted. This causes large increasing emitter current result in breakdown such breakdown is called as punch through (or) reach through.