

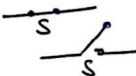
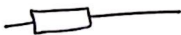


Electric Circuits

+

Component	Real shape	Symbol
Battery		
Switch		
Lamp		
Resistor	-	
Heater	-	
Bell	-	

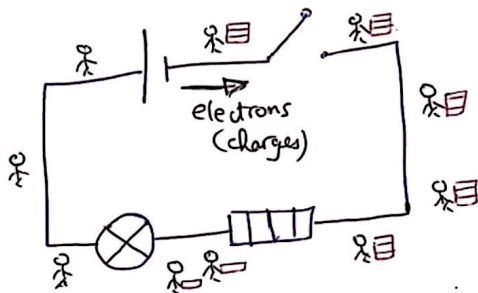

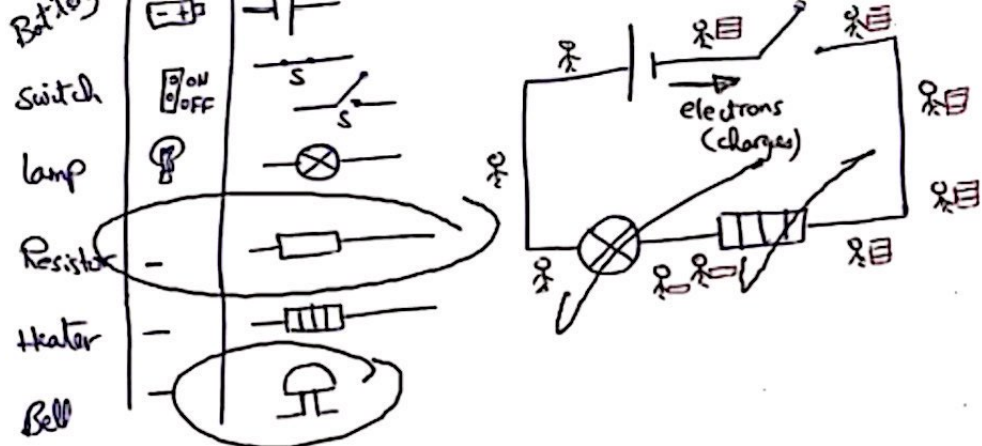

(I)
A) Electric current - The amount of charge flowing per second

- units: Ampere (A) - opposite to direction of electrons.

$$I = \frac{Q}{t}$$

Current (A) ← I = $\frac{Q \rightarrow \text{charge (Coulomb)}}{t \rightarrow \text{time (s)}}$

(V)
B) Volt : $V \text{ or } V = \frac{E \text{ or } J}{Q \text{ or } C}$

→ Electromotive force : amount of energy gained by each unit charge.
 * e.m.f. *


→ potential difference : amount of energy lost by each unit charge.

○ Resistance : it's a measure of the difficulty to pass electricity
 - units: ohms (Ω)

Measuring Devices


Voltmeter — V —

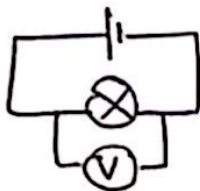- measures volt
- units: V, KV, mV
- Connected in parallel



Ammeter — A —

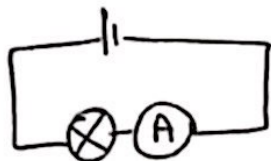- measures current
- units: A, KA, mA
- Connected in series




Ohm's law

$$V = I \times R$$


V
I R

$$I = \frac{V}{R} \quad R = \frac{V}{I}$$


Ex.

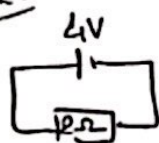

$I =$

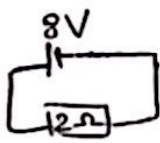

$I =$

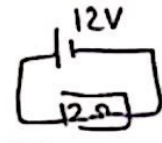

$I =$

* For constant 'R',

V and I are -----


$V \uparrow$

Ohm's Law


$$V = I \times R$$

$$I = \frac{V}{R} \quad R = \frac{V}{I}$$



Ex:

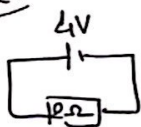

$$I = \text{?}$$

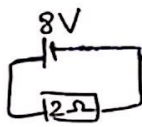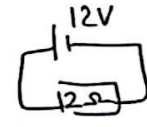


$$I = \text{?}$$




$$I = \text{?}$$

* For constant 'R',


V and I are -----

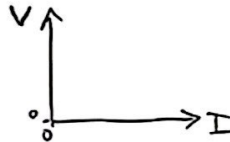


Ex:

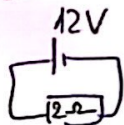

$$I = \text{?}$$

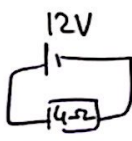

$$I = \text{?}$$

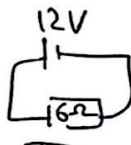

$$I = \text{?}$$


* For constant 'V',

I and R are



V-I relationship:

* Constant Resistance

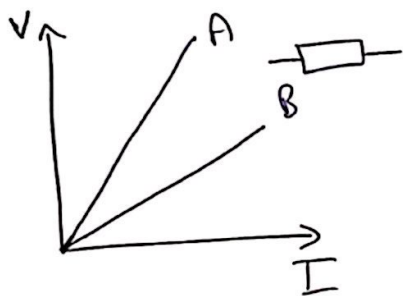


- Slope =
- Resistance is constant
- Higher Resistance
↳ closer to volt axis




- Resistance increases
- because temperature increases
- bends towards volt axis

- Slope =
- Resistance is constant
- Higher Resistance
↳ closer to volt axis
- Resistance increases
- because temperature increases
- bends towards Volt axis

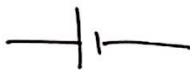* Describe How to measure the Resistance of lamp?



* Power;

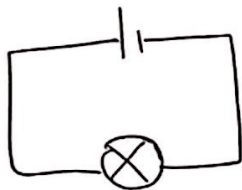

$$P = \begin{cases} I \times V \\ I^2 \times R \\ \frac{V^2}{R} \end{cases}$$


$\int_{\text{watt}}$

* $\text{Energy} = P \times t$

$\swarrow \quad \quad \quad \downarrow \quad \quad \quad \searrow$


J Watt Sec.

* Factors affecting Resistance of wire:-

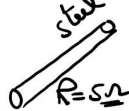


1) Material Resistivity (ρ) ($R \propto \rho$)

2) length

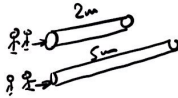

($R \propto L$) $20\Omega \xrightarrow[L \times 2]{R \times 2} 40\Omega$

3) Cross-sectional Area.

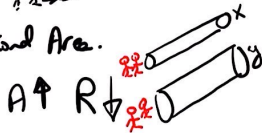

($R \propto \frac{1}{A}$)
 $A \uparrow R \downarrow$


$20\Omega \xrightarrow[R \div 2]{A \times 2} 10\Omega$

4) Temp. $\uparrow$

($T \uparrow R \uparrow$)

÷ Types of Connections

Series

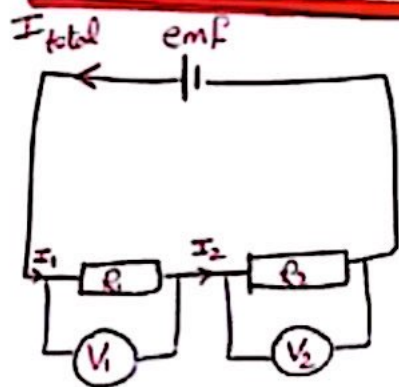

$$1) I_{total} = I_1 = I_2$$

- Current is same


$$2) EmF = V_1 + V_2$$

- Volt is divided

- Component with more 'R' gets more 'V'

$$3) R_{total} = R_1 + R_2$$

parallel

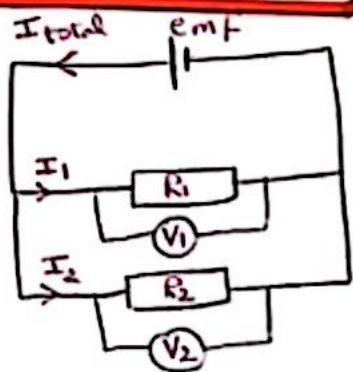

$$1) I_{total} = I_1 + I_2$$

- Current is divided

- branch with more 'R' gets less 'I'

$$2) EmF = V_1 = V_2$$


- Volt is the same

$$3) R_{total} = \frac{R_1 \times R_2}{R_1 + R_2} \rightarrow \text{for 2 Resistors}$$

$$\left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right]^{-1}$$

⇒ General Rule

Ex:

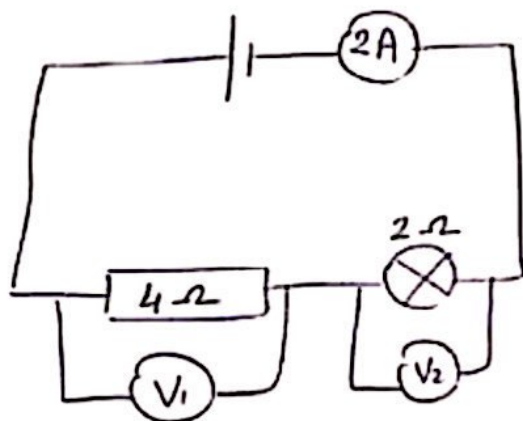


a) $V_1 =$

b) $V_2 =$

c) $\text{emf} =$

d) $R_{\text{total}} =$

Ex 8

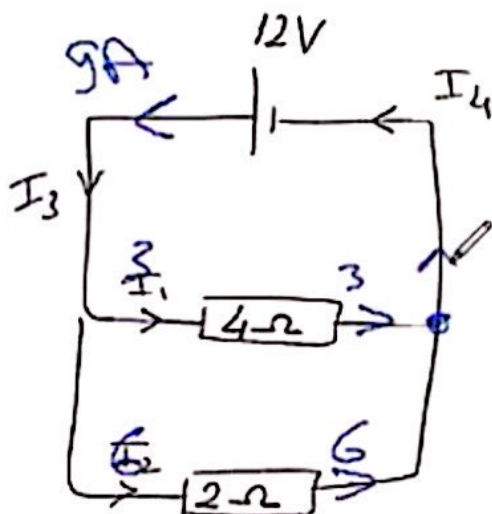

a) $I_1 =$


c) $I_3 =$

b) $I_2 =$


d) $I_4 =$

e) $P_{total} =$

Variable Resistor (Rheostat)

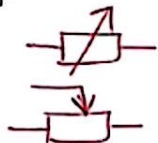


Exs

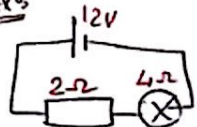


$$I =$$

$$V_{\text{lamp}} =$$

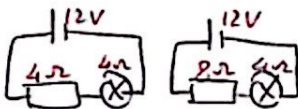



$$I =$$

$$V_{\text{lamp}} =$$

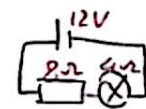

$$I =$$

$$V_{\text{lamp}} =$$

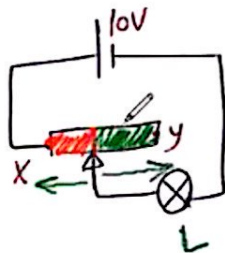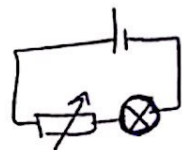


* Summary:-

- If you want to increase the brightness of lamp, put it in series to smaller Resistance.

- potential divider

Fixed Variable

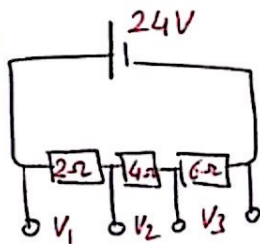


$$I =$$

$$V_1 =$$

$$V_2 =$$

$$V_3 =$$

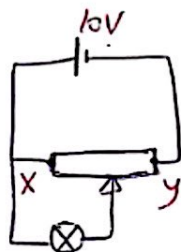

* Summary:-

- If you want to increase the brightness of the lamp, put it in parallel to larger Resistance.

House (Mains) Electricity -


Hazards of over-current:

- 1- overheating / Melting of wires
- 2- Firing
- 3- Damage of Devices (Appliances)

* How to avoid { use thicker cables
Fuse / Circuit breaker






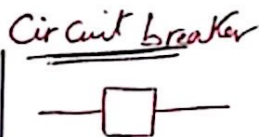
- every Fuse has a Rating (e.g. 10A)
- it melts if current exceeds this rating



- Contains Electromagnet
- Re-usable.

How to Control Brightness of lamp? (Current in Circuit)


Variable Resistor (Rheostat)

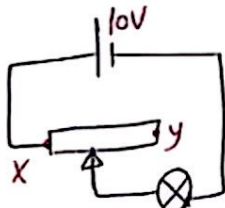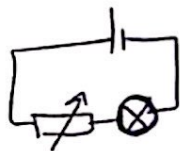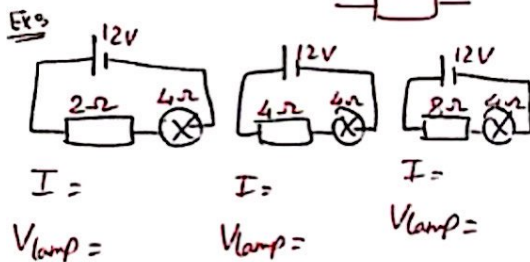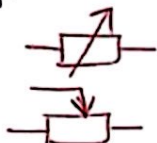


Potential Divider

Fixed


Variable

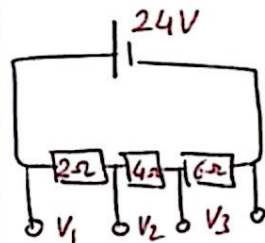

$I =$
 $V_1 =$
 $V_2 =$
 $V_3 =$

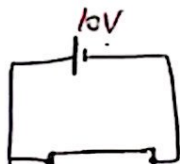

Ex.

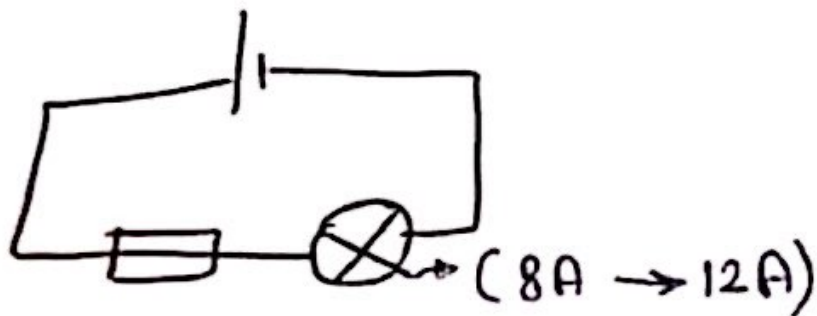


$(5A, 10A, 15A)$

types of power sources

Direct Current
'D.C.'

- Current flows in one direction.

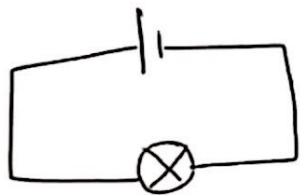

Alternating Current
'A.C.'

- Reverses direction of current every cycle.

