

Current electricity

Electric current

$$I = \frac{\text{Charge (q)}}{\text{Time (t)}} \quad \text{as } q = ne$$

$$I = \frac{ne}{t}$$

1 ampere =  $\frac{1 \text{ coulomb}}{1 \text{ second}}$

→ Current in domestic appliance = 1 A  
 → Current carried by lightning =  $10^4 \text{ A}$   
 → Current in our nerves =  $10^{-6} \text{ A} = 1 \mu\text{A}$

Period of revol<sup>n</sup> of  $e^-$

$$T = \frac{2\pi r}{v}$$

Frequency of revolution

$$v = \frac{1}{T} = \frac{v}{2\pi r}$$

Current (I) = Charge flowing in 1 revol<sup>n</sup> × No. of revol<sup>n</sup> per second.

$$I = ev = \frac{ev}{2\pi r}$$

Electric charge → coulomb  
 Current → Ampere

Electromotive force (emf)

$$\text{emf} = \frac{\text{Work done}}{\text{charge}}$$

5) Ohm's Law (in conduction)

$$R = \frac{V}{I} \quad \text{or } V = IR$$

1 ohm =  $\frac{1 \text{ volt}}{1 \text{ ampere}}$

Factor affecting the resistance

- Length ( $R \propto l$ )
- Area of cross sect<sup>n</sup> ( $R \propto \frac{1}{A}$ )
- Nature of material ( $R = \rho \frac{l}{A}$ )

∴  $R = \rho$   
 S.I. unit of  $\rho$  = ohm meter ( $\Omega m$ )

6) Resistivity or specific resistance

$$\rho = \frac{RA}{l}$$

7) Conductance (G)

$$G = \frac{1}{R}$$

→ ohm<sup>-1</sup>

8) Conductivity =  $\frac{1}{\text{Resistivity}}$

→ ohm<sup>-1</sup>m

9) Current density

$$j = \frac{\text{Current}}{\text{Area}}$$

③ \* Current electricity \*

① Electric current

$$I = \frac{\text{charge (q)}}{\text{Time (t)}} \quad \hookrightarrow \text{as } q = ne$$


$$I = \frac{ne}{t}$$

1 ampere =  $\frac{1 \text{ coulomb}}{1 \text{ second}}$

- Current in domestic appliance = 1 A ✓
- Current carried by lightning =  $10^4$  A ✓
- Current in our nerves =  $10^{-6}$  A = 1  $\mu$ A ✓

② Period of revol<sup>n</sup> of e<sup>-</sup>

$$T = \frac{2\pi r}{v}$$

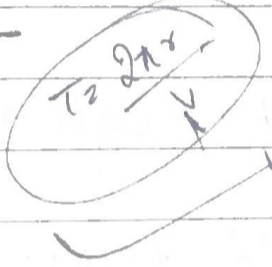

③ Frequency of revolution

$$v = \frac{1}{T} = \frac{v}{2\pi r}$$

• Current (I) = Charge flowing in 1 revol<sup>n</sup> × No. of revol<sup>n</sup> per second.

$$I = ev = \frac{ev}{2\pi r}$$


electric charge → coulomb.  
current → Ampere.

④ Electromotive force (emf)

$$\text{emf} = \frac{\text{work done}}{\text{charge}}$$

⑤ Ohm's Law (At const. temp)
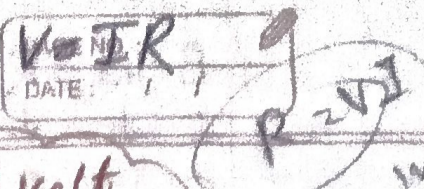
$$R = \frac{V}{I} \quad \text{or} \quad V = IR$$



1 ohm =  $\frac{1 \text{ volt}}{1 \text{ ampere}}$

⑥ Factor affecting the resistance

- ① length ( $R \propto l$ )
- ② Area of cross sect<sup>n</sup> ( $R \propto \frac{1}{A}$ )

- ③ Nature of material ( $R = \rho \frac{l}{A}$ )

$$\therefore R = \rho$$

S.I. unit of  $\rho$  = ohm meter ( $\Omega m$ )

⑥ Resistivity or specific resistance

$$\rho = \frac{RA}{l}$$

⑦ Conductance (G)

$$G = \frac{1}{R}$$

$\hookrightarrow M L^{-2} T^3 A^2$   
ohm<sup>-1</sup>

⑧ Conductivity =  $\frac{1}{\text{Resistivity}}$

⑨ Current density

$$\hookrightarrow = \frac{\text{current}}{\text{Area}}$$

Colour code - *Black, Brown, Red, Orange, Yellow, Green, Blue, Violet, Grey, White*

used to find resistance value of carbon resistor & its % accuracy

B B R O Y of  $10^0$   $10^1$   $10^2$   $10^3$   $10^4$   $10^9$

Some extra colour - Gold  $\rightarrow$  5%  
 Silver  $\rightarrow$  10%  
 No fourth band  $\rightarrow$  20%

10) Accelerat<sup>n</sup> =  $\frac{\text{force}}{\text{mass}}$

16) Temperature Dependence  
 $T_2 > T_1$   
 $R_T = R_0 (1 + \alpha \Delta T)$   $\alpha = k^{-1}, e^{-1}$

11) Drift Velocity  $v_d = \frac{e E \tau}{m}$   
 electric field, relax<sup>n</sup> time, mass of elect<sup>n</sup>

For metals  $\rightarrow$  Resistance ( $\uparrow$ ) w/ temp  
 $\therefore$  temp. coefficient ( $\alpha$ )

12) Current in terms of Drift velocity  
 $I = neAv_d$

$\alpha = \frac{R_2 - R_1}{R_1(t_2 - t_1)}$   
 $t_1 = 0^\circ C, t_2 = 1^\circ C$

13) Current density  
 $j = env_d$

$E_g < 1\text{eV}$  (semiconductor) at room temp  
 $E_g \geq 1\text{eV}$  (insulator) at room temp

Avogadro's no. =  $6.023 \times 10^{23} \text{ mol}^{-1}$   
 $e = 1.6 \times 10^{-19} \text{ C}$

14) Relaxat<sup>n</sup> time ( $\tau$ )  
 $\tau = \frac{ml}{ne^2 EA}$   $10^{-14} \text{ s}$

17) Power  $\rightarrow P = I^2 R$   
 electric energy  $\rightarrow W = VIT$

$1 \text{ kWh} = 3.6 \times 10^6 \text{ J}$

15) Mobility ( $\mu$ )  
 $\mu = \frac{v_d}{E}$   
 Drift velocity, electric field

(18) Combinat<sup>n</sup> of Resistors

(i) In series → current same  
→ voltage divides  
 $R_{eq} = R_1 + R_2 + R_3$   $R_1 + R_2$

(ii) In parallel → Voltage same  
→ current divides  
 $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$

(\*) Resistances are in ohm ( $\Omega$ )

→ for 2 resistances in parallel  
 $I_1 = \frac{R_2 I}{R_1 + R_2}$  &  $I_2 = \frac{R_1 I}{R_1 + R_2}$

(19) Internal Resistance, Terminal P.d.

∴ Terminal voltage →  
 $V = \mathcal{E} - Ir$

∴ Terminal p.d. when cell being charged  
 $V = \mathcal{E} + Ir$

(20) Terminal p.d. of cell

$$V = IR = \frac{\mathcal{E}R}{R+r}$$

(21) Internal resistance of a cell

$$r = R \left[ \frac{\mathcal{E} - V}{V} \right]$$

$$\rho = R$$

D.F. →  $[ML^3T^{-3}A^{-2}]$

(22) Grouping of cells

(i) For 'n' cells in series  
 $I = \frac{n\mathcal{E}}{R+nR}$   
 $I = \frac{n\mathcal{E}}{R+nR}$

(ii) For 'n' cells in parallel  
 $I = \frac{n\mathcal{E}}{nR+r}$  no. of cells.  
 $I = \frac{n\mathcal{E}}{nR+r}$

(iii) Mixed grouping  
 $I = \frac{mn\mathcal{E}}{mR+nR}$   
no. of row of cells

(23) Heating effect of current  
 $H = I^2 R t$   
 $H = I^2 R t$

(24) Electric power  
 $P = \frac{W}{t}$   
 $P = \frac{W}{t}$

(25) Kirchhoff's law

(i) Junct<sup>n</sup> rule  
 $\sum I = 0$  or  $I_1 + I_2 = I_3 + I_4$

(ii) Loop Rule  
 $\sum V = 0$

\* Current is a scalar quantity  
bcz of dot product

26 Potentiometer [Vol]   
 (i) emf of 2 cells :-   
 $\frac{E_1}{E_2} = \frac{l_1}{l_2}$    
 based on null error   
 Not force   
 max<sup>m</sup> p.d b/w 2 electrodes

(ii) internal resist. of cell.

$$r = \frac{l_1 - l_2}{l_2} \times R$$

(iii) Potential gradient:

$$k = \frac{V}{L}$$

27 Wheat Stone bridge

$$\frac{P}{Q} = \frac{R}{S}$$

At balance  $\rightarrow$  (Circuit) current = zero.

Unknown R  $\Rightarrow S = \frac{Q}{P} \times R$

$\therefore$  Resistance per unit length

$$S = \frac{R(100-L)}{L}$$

28 Resistivity ( $\rho$ )

$$\rho = \frac{SA}{L} = \frac{S \times \pi r^2}{L}$$

29 Meter bridge

$$\frac{R}{X} = \frac{L}{100-L}$$

$S = \frac{(100-l)}{L} \times R$  balancing length.

Series combination  $\rightarrow$  Resistors connects end to end

PAGE NO.:   
 DATE: / /

Parallel combination  $\rightarrow$  Resistors connected side by side.



Rel<sup>n</sup> b/w current density & drift velocity

$$\vec{J} = n e v_d$$
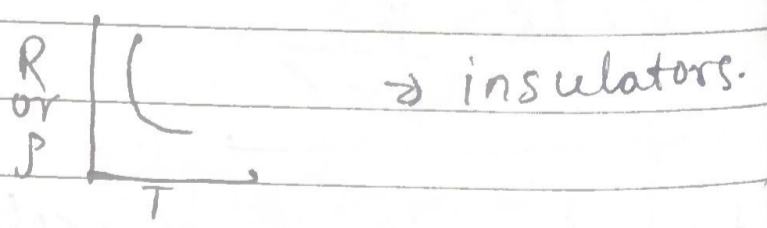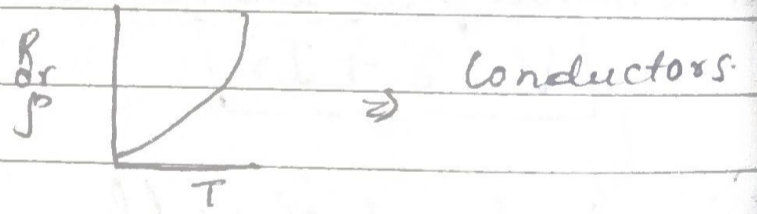
# Microscopic ohm's law / ( $\sigma$ ),  $J$ ,  $E$  Rel<sup>n</sup>.

$$\vec{J} = \sigma \vec{E}$$

$\alpha$  (temp. coefficient)   
 $\alpha$  (ve) for Ag, Cu etc.



Ohm's law

